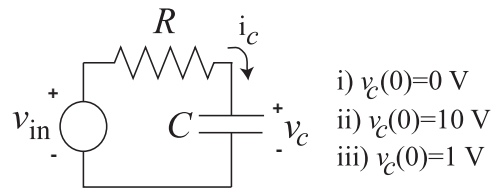



**Due:** Monday April 29, 2002

**Problem 1:**


For each of the circuits below, derive the differential equation which relates input to output, and solve for the unit step response for the listed initial conditions. Note that some of the circuits use a current source input. In each case, make a sketch of the output vs. time.




1. Solve for  $i_c$  as output

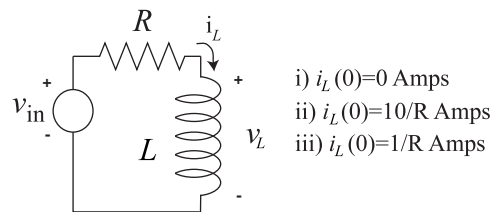

2. Solve for  $v_L$  as output

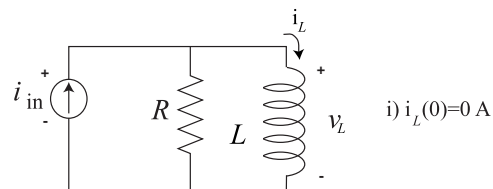


3. Solve for  $v_L$  as output

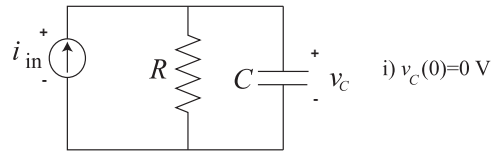

4. Solve for  $v_c$  as output

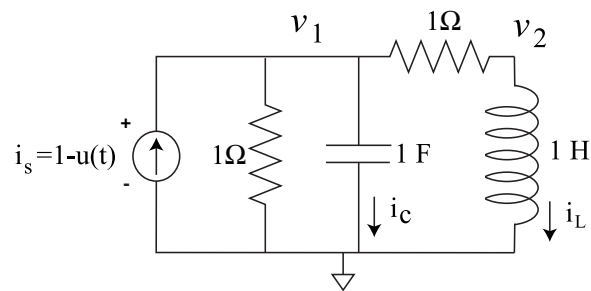**Problem 2:** This problem studies the circuit shown below.



1. For  $t < 0$ , what are the values of  $v_1$ ,  $v_2$ ,  $i_L$ , and  $i_c$
2. What are the initial conditions at  $t = 0^+$ , i.e., the values of  $v_1(0^+)$  and  $\frac{dv_1}{dt}(0^+)$ ? Be sure to show how you derived these results.
3. For  $t \geq 0$  a differential equation describing this circuit in terms of  $v_1$  is

$$\frac{d^2 v_1}{dt^2} + 2 \frac{dv_1}{dt} + 2v_1 = 0.$$

Write the solution of this equation as a function of time for  $T \geq 0$ . Show carefully how you derived the solution and satisfied the initial conditions from the previous section. If you were not able to derive the initial conditions, you can write your solution in terms of  $v_1(0^+)$  and  $\frac{dv_1}{dt}(0^+)$ .